

HW6 : SystemC AMS Modeling - ELN

Student Name: Amirhosein Yavarikhoo

Student ID: 810199514

Abstract— SystemC AMS offers us a solution to connect digital circuits to analog circuits. In this experiment, we use a systemC module to create a DE sin signal, convert it to analog, filter it using a bandpass filter and at last convert it again to digital.

Keywords— System C modelling, analog circuits, digital to analog converters, bandpass filter

I. INTRODUCTION

In this assignment, we design a bandpass filter and connect it to a simple sin wave generator that is digital and see how the filter works.

II. BANDPASS FILTER

Bandpass filter with two converters for digital to analog signals is shown below:

```
1 #include <systemc.h>
2 #include <systemc-ams.h>
3 SC_MODULE(MyFilter) {
4 public:
5     sc_in<double> in;
6     sc_out<double> out;
7     sca_eln::sca_de_vsource Vin;
8     sca_eln::sca_r *R1;
9     sca_eln::sca_r *Rload;
10    sca_eln::sca_c *C1;
11    sca_eln::sca_c *C2;
12    sca_eln::sca_node a;
13    sca_eln::sca_node b;
14    sca_eln::sca_node c;
15    sca_eln::sca_node_ref gnd;
16    MyFilter(sc_module_name): Vin("Vin"), Vout("Vout") {
17        R1 = new sca_eln::sca_r("r1", 200);
18        R1->n(a);
19        R1->p(b);
20        R1->set_timestep(1, SC_MS);
21        Rload = new sca_eln::sca_r("rload", 1000);
22        Rload->n(c);
23        Rload->p(gnd);
24        C1 = new sca_eln::sca_c("c1", 2.5e-6);
25        C1->n(b);
26        C1->p(gnd);
27        C2 = new sca_eln::sca_c("c2", 1e-6);
28        C2->n(b);
29        C2->p(c);
30        Vin.p(a);
31        Vin.n(gnd);
32        Vin.inp(in);
33        Vin.set_timestep(1, SC_MS);
34        Vout.p(c);
35        Vout.n(gnd);
36        Vout.outp(out);
37    }
38 }
39
40
```

Fig. 1 bandpass filter code

III. SIN WAVE GENERATOR

To create a sin wave, we use a simple SC_THREAD and a for loop.

```
1 #include <systemc.h>
2 #include <systemc-ams.h>
3 SC_MODULE(Sinus) {
4     sc_out<double> out;
5     SC_CTOR(Sinus) {
6         SC_THREAD(generate);
7     }
8     void generate() {
9         for (int i = 0; i < 2000; i++) {
10             out->write(sin(2 * 3.14 * 100 * i));
11             wait(0.1, SC_MS);
12         }
13     }
14 }
```

Fig. 2 Sin wave generator

IV. TESTBENCH

Code for testbench is shown below:

```
1 #include "MyFilter.cpp"
2 #include "Sin.cpp"
3 SC_MODULE(TB) {
4     sc_signal<double> in, out;
5     MyFilter* UUT;
6     Sinus* input_wave;
7     SC_CTOR(TB) {
8         input_wave = new Sinus("wave_instance");
9         input_wave->out(in);
10        UUT = new MyFilter("filter_instance");
11        UUT->in(in);
12        UUT->out(out);
13    }
14 }
```

Fig. 3 Testbench code

Output of the sin wave generator connects to the input of the bandpass filter.

Main function is shown below:

```
1 #include "TB.cpp"
2
3 int sc_main(int argc, char* argv[]) {
4     sc_set_time_resolution(0.01, SC_MS);
5
6     TB* testbench = new TB("testbench_instance");
7     sc_trace_file* HW6 = sc_create_vcd_trace_file("HW6");
8     sc_trace(HW6, testbench->in, "vin");
9     sc_trace(HW6, testbench->out, "vout");
10
11     sc_start(500, SC_MS);
12     return 0;
13 }
```

Fig. 4 main function

